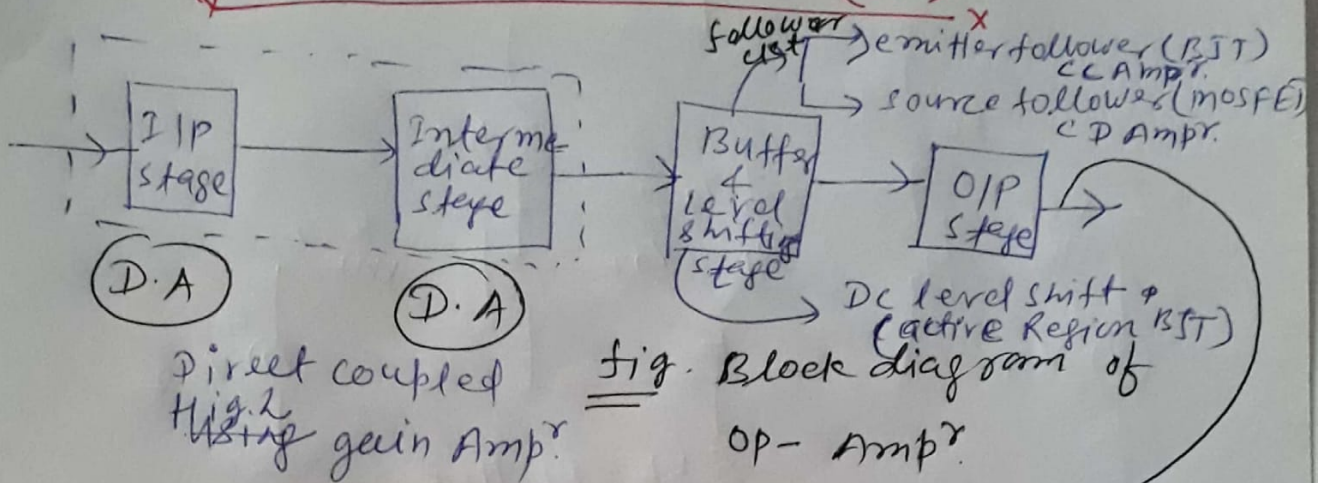


Differential Amplifier (Op)



push-pull Amp^r (class-B).

- (i) High o/p voltage.
- (ii) High current swing capability.
- (iii) Low power dissipation
- (iv) short ckt protection.

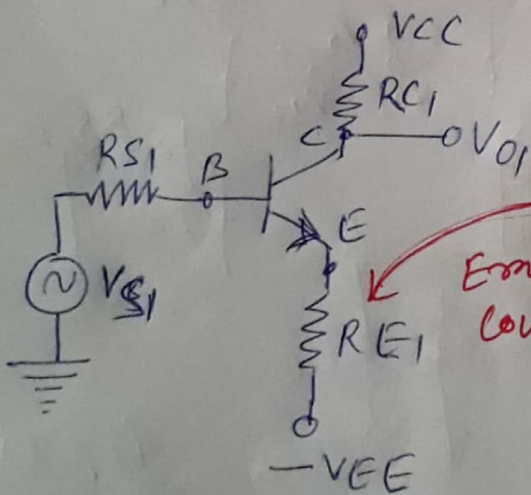


fig (C.E. Amp^r)



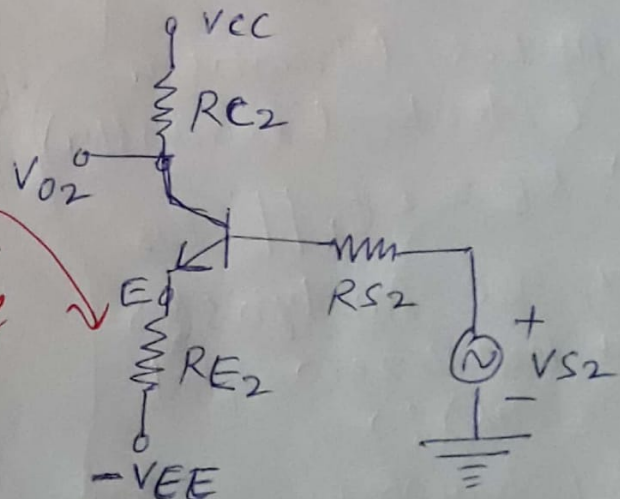


fig C.E. Amp^r

Emitter coupling

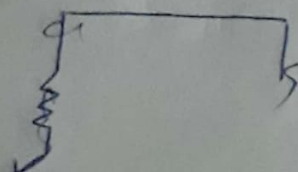After coupling of Emitter terminal, the New ckt for differential Amp^r is



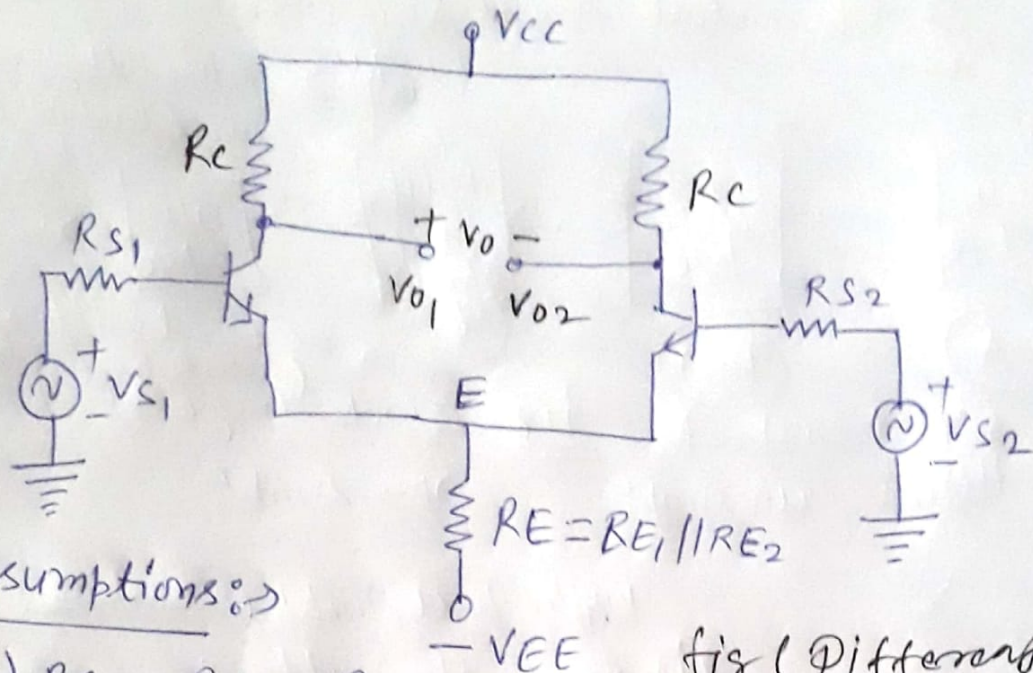

Assumptions: \Rightarrow

- (i) $R_{C1} = R_{C2} = R_C$
- (ii) $R_{S1} = R_{S2} = R_S$
- (iii) $|V_{CC}| = |-V_{EE}|$
- (iv) $\beta_1 = \beta_2 = \beta$
- (v) Matched transistor (identical transistor)
- (vi) $R_E = R_{E1} || R_{E2}$

fig (Differential Amp)

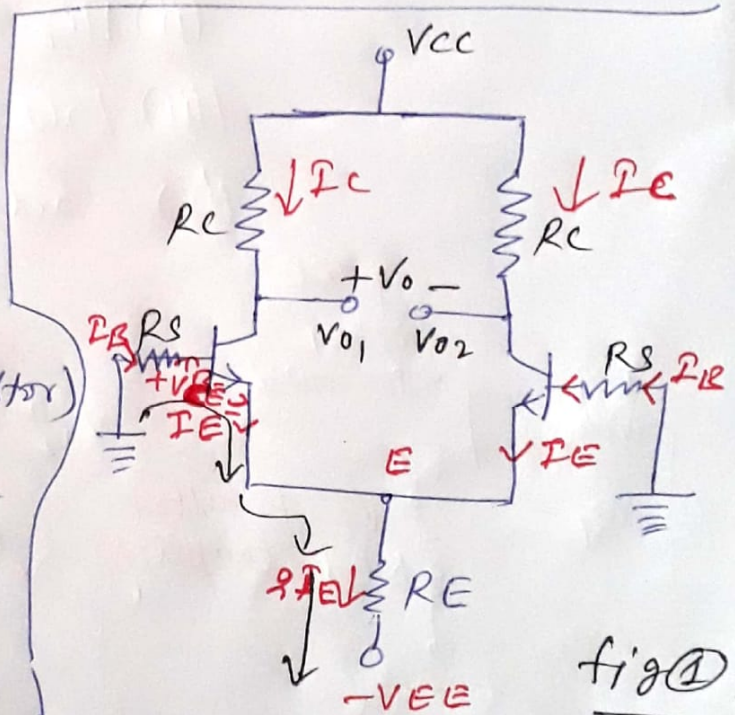


fig 1

Now, DC Analysis \Rightarrow
 (that means zero signal analysis) \Rightarrow

Calculation of Differential Amp: - fig 1

Now, Apply KVL,

$$I_B R_S + V_{BE} + 2 R_E I_E - V_{EE} = 0 \quad \text{--- (1)}$$

$$I_B + I_C = I_E$$

$$\beta = \frac{I_C}{I_B}$$

$$\beta I_B + I_B = I_E$$

$$(\beta + 1) I_B = I_E \quad \downarrow \downarrow$$

In transistor have two operating points.
 (i) $I_C Q \rightarrow$ collector current Q point.

(ii) $V_{CE} Q.$

operating points.

Now, change eq (1), then

$$I_B R_S + V_{BE} + 2 R_E I_E - V_{EE} = 0$$

$$I_B R_S + V_{BE} + 2 R_E I_B (1 + \beta) - V_{EE} = 0$$

$$I_B [R_S + 2 R_E (1 + \beta)] = V_{EE} - V_{BE}$$

$$\frac{I_C}{\beta} [R_S + 2 R_E (1 + \beta)] = V_{EE} - V_{BE} \quad \because I_B = \frac{I_C}{\beta}$$

$$I_C = \frac{V_{EE} - V_{BE}}{\frac{R_S}{\beta} + \frac{2 R_E (1 + \beta)}{\beta}}$$

operating point of transistor.

or.

$$I_{CQ} = \frac{V_{EE} - V_{BE}}{\frac{R_S}{\beta} + 2 R_E}$$

if suppose,

$$\frac{R_S}{\beta} \ll 2 R_E, \text{ then}$$

or

$$R_S = 0$$

$$\therefore I_{CQ} = \frac{V_{EE} - V_{BE}}{2 R_E}$$

* if given,

$$V_{CC} = 10V$$

$$-V_{EE} = -10V$$


$$V_{BE} = 0.7V$$

$$R_E = 1k\Omega$$

$$\therefore I_{CQ} = \frac{10 - 0.7}{2 \times 1}$$
$$= \frac{9.3}{2}$$

$$I_{CQ} = 4.65 \text{ mA}$$

Ans

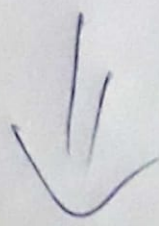

DC Analysis of zero signal analysis:-

(ii) Apply KVC,

$V_{CB} = V_{CE} = V_C - V_E$

$V_{CC} = I_E R_C + V_C$ (1)

$V_C = V_{CC} - I_E R_C$

$V_{CE} = V_{CC} - I_C R_C - V_E$ (2)

$I_B R_S + V_{BE} + V_E = 0$

$I_B R_S < V_{BE}$


$I_B R_S < 0.7V$

$V_{BE} + V_E = 0$

$V_E = -V_{BE}$

$V_{CE} = V_{CC} - I_C R_C + V_{BE}$

Q-point
2nd operating point

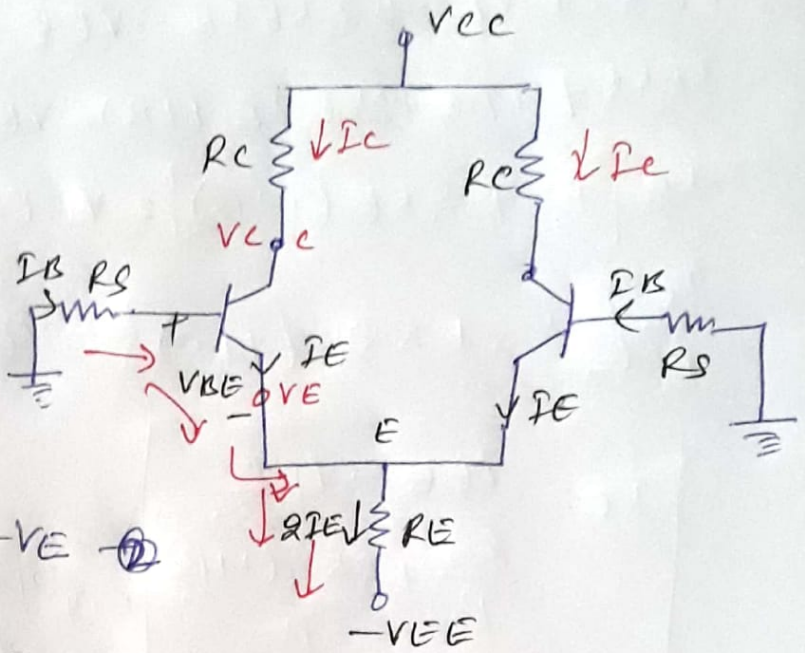

Now, change eq (1), then

$$I_B R_S + V_{BE} + 2 R_E I_E - V_{EE} = 0$$

$$I_B R_S + V_{BE} + 2 R_E I_B (1 + \beta) - V_{EE} = 0$$

$$I_B [R_S + 2 R_E (1 + \beta)] = V_{EE} - V_{BE}$$

$$\frac{I_C}{\beta} [R_S + 2 R_E (1 + \beta)] = V_{EE} - V_{BE} \quad \because I_B = \frac{I_C}{\beta}$$

$$I_C = \frac{V_{EE} - V_{BE}}{\frac{R_S}{\beta} + \frac{2 R_E (1 + \beta)}{\beta}}$$

operating point of transistor.

or.

$$I_{CQ} = \frac{V_{EE} - V_{BE}}{\frac{R_S}{\beta} + 2 R_E}$$

if suppose,

$$\frac{R_S}{\beta} \ll 2 R_E, \text{ then}$$

or

$$R_S = 0$$

$$\therefore I_{CQ} = \frac{V_{EE} - V_{BE}}{2 R_E}$$

* if given,

$$V_{CC} = 10V$$

$$-V_{EE} = -10V$$

$$V_{BE} = 0.7V$$

$$R_E = 1k\Omega$$

$$\therefore I_{CQ} = \frac{10 - 0.7}{2 \times 1}$$

$$= \frac{9.3}{2}$$

$$I_{CQ} = 4.65 \text{ mA} \quad \underline{\text{Ans}}$$

