

Finite State Machines

Introduction

Finite State Machines (FSM) are sequential circuit used in many digital systems to control the behavior of systems and dataflow paths. Examples of FSM include control units and sequencers. This lab introduces the concept of two types of FSMs, Mealy and Moore, and the modeling styles to develop such machines. *Please refer to the Vivado tutorial on how to use the Vivado tool for creating projects and verifying digital circuits.*

Objectives

After completing this lab, you will be able to:

- Model Mealy FSMs
- Model Moore FSMs

Mealy FSM


Part 1

A finite-state machine (FSM) or simply a state machine is used to design both computer programs and sequential logic circuits. It is conceived as an abstract machine that can be in one of a finite number of user-defined states. The machine is in only one state at a time; the state it is in at any given time is called the *current state*. It can change from one state to another when initiated by a triggering event or condition; this is called a *transition*. A particular FSM is defined by a list of its states, and the triggering condition for each transition.


The behavior of state machines can be observed in many devices in modern society performing a predetermined sequence of actions depending on a sequence of events with which they are presented. Simple examples are vending machines which dispense products when the proper combination of coins are deposited, elevators which drop riders off at upper floors before going down, traffic lights which change sequence when cars are waiting, and combination locks which require the input of combination numbers in the proper order.

The state machines are modeled using two basic types of sequential networks- Mealy and Moore. In a Mealy machine, the output depends on both the present (current) state and the present (current) inputs. In Moore machine, the output depends only on the present state.

A general model of a Mealy sequential machine consists of a combinatorial network, which generates the outputs and the next state, and a state register which holds the present state as shown below. The state register is normally modeled as D flip-flops. The state register must be sensitive to a clock edge. The other block(s) can be modeled either using the `always` procedural block or a mixture of the `always` procedural block and dataflow modeling statements; the `always` procedural block will have to be sensitive to all inputs being read into the block and must have all output defined for every branch in order to model it as a combinatorial block. The two blocks Mealy machine can be viewed as

 

 Here are the state diagram of a parity checker Mealy machine and the associated model.



```

type state_type is (S0, S1);
signal state, next_state : state_type;

```

```
begin
```

```
SYNC_PROC : process (clk)
```

```
begin
```

```
  if rising_edge(clk) then
```

```
    if (reset = '1') then
```

```
      state <= S0;
```

```
    else
```

```
      state <= next_state;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

```
NEXT_STATE_DECODE : process (state, x)
```

```
begin
```

```
  parity <= '0';
```

```
  case (state) is
```

```
    when S0 =>
```

```
      if (x = '1') then
```

```
        parity <= '1';
```

```
        next_state <= S1;
```

```
      else
```

```
        next_state <= S0;
```

```
      end if;
```

```
    when S1 =>
```

```
      if (x = '1') then
```

```
        next_state <= S0;
```

```
      else
```

```
        parity <= '1';
```

```
        next_state <= S1;
```

```
      end if;
```


```
    when others =>
```

```
      next_state <= S0;
```

```
  end case;
```

```
end process;
```

 The three blocks Mealy machine and the associated model are shown below.



```
type state_type is (S0, S1);
signal state, next_state : state_type;


begin

SYNC_PROC : process (clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            state <= S0;
        else
            state <= next state;
        end if;
    end if;
end process;


OUTPUT_DECODE : process (state, x)
begin
    parity <= '0';
    case (state) is
        when S0 =>
            if (x = '1') then
                parity <= '1';
            end if;
        when S1 =>
            if (x = '0') then
                parity <= '1';
            end if;
        when others =>
            parity <= '0';
        end case;
end process;

NEXT_STATE_DECODE : process (state, x)
begin
    next_state <= S0;
    case (state) is
        when S0 =>
            if (x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
        end case;
end process;
```

The state assignments can be of one-hot, binary, gray-code, and other types. Usually, the synthesis tool will determine the type of the state assignment, but user can also force a particular type by changing the synthesis property as shown below. The state assignment type will have an impact on the number of bits used in the state register; one-hot encoding using maximum number of bits but decodes very fast to compact (binary) encoding using smallest number of bits but taking longer to decode.

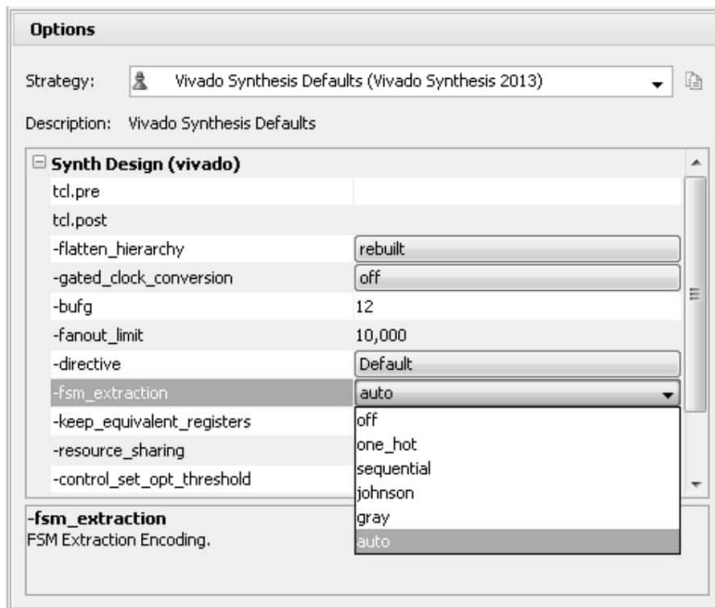

 
1-1. Design a sequence detector implementing a Mealy state machine using three always blocks. The Mealy state machine has one input (a_{in}) and one output (y_{out}). The output y_{out} is 1 if and only if the total number of 1s received is divisible by 3 (hint: 0 is inclusive, however, reset cycle(s) do not count as 0- see in simulation waveform time=200). Develop a testbench and verify the model through a behavioral simulation. Use SW15 as the clock input, SW0 as the a_{in} input, the BTNU button as reset input to the circuit, number of 1s count on LED7:LED4, and LED0 as the y_{out} output. Go through the design flow, generate the bitstream, and download it into the Basys3 or the Nexys4 DDR board. Verify the functionality.




Moore FSM

 Part 2

A general model of a Moore sequential machine is shown below. Its output is generated from the state register block. The next state is determined using the present (current) input and the present (current) state. Here the state register is also modeled using D flip-flops. Normally Moore machines are described using three blocks, one of which must be a sequential and the other two can be modeled using `always` blocks or a combination of `always` and dataflow modeling constructs.



 Here is the state graph of the same parity checker to be modeled as a Moore machine. The associate model is shown below.



```

type state_type is (S0, S1);
signal state, next_state : state_type;

```

```
begin
```

```

SYNC_PROC : process (clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            state <= S0;
        else
            state <= next_state;
        end if;
    end if;
end process;

```

```

OUTPUT_DECODE : process (state)
begin
    case (state) is
        when S0 =>
            parity <= '0';
        when S1 =>
            parity <= '1';
        when others =>
            parity <= '0';
    end case;
end process;


```

```

NEXT_STATE_DECODE : process (state, x)
begin
    next_state <= S0;
    case (state) is
        when S0 =>
            if (x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
    end case;
end process;

```

 
- 2-1. Design a sequence detector implementing a Moore state machine using three always blocks. The Moore state machine has two inputs ($ain[1:0]$) and one output ($yout$). The output $yout$ begins as 0 and remains a constant value unless one of the following input sequences occurs:
- (i) The input sequence $ain[1:0] = 01, 00$ causes the output to become 0
 - (ii) The input sequence $ain[1:0] = 11, 00$ causes the output to become 1
 - (iii) The input sequence $ain[1:0] = 10, 00$ causes the output to toggle.
- Develop a testbench (similar to the waveform shown below) and verify the model through a behavioral simulation. Use SW15 as the clock input, SW1-SW0 as the $ain[1:0]$ input, the BTNU button as reset input to the circuit, and LED0 as the $yout$ output. Go through the design flow, generate the bitstream, and download it into the Basys3 or the Nexys4 DDR board. Verify the functionality.




Mealy FSM Using ROM

 Part 3

A Mealy sequential machine can also be implemented using a ROM memory as shown below. The ROM memory holds the next state and output content. The external inputs and the current state form the address input to the ROM. The ROM typically is implemented using LUTs instead of Block RAM since LUTs give a better utilization ratio resulting from a smaller number of states in a design.



 - 3-1. Design a specific counts counter (counting sequence listed below) using ROM to develop a Mealy state machine. Develop a testbench and verify the model through behavioral simulation. Use SW15 as the clock input, the BTNU button as reset input to the circuit, and LED2:LED0 as the count output of the counter. Go through the design flow, generate the bitstream, and download it into the Basys3 or the Nexys4 DDR board. Verify the functionality.
- The counting sequence will be: 000, 001, 011, 101, 111, 010 (repeat) 000, ...



Conclusion

In this lab, you learned Mealy and Moore state machine modeling methodologies. You designed and implemented sequence detector, a sequence generator, and code converters using the two and three always blocks styles.