

111


unit-2
Lecture-6

07/04/2020

MicroWave Engineering
EC - 6th sem (3rd year)

Faculty Incharge :- Shobhit Saxena

ABCD Parameters for Cascaded Network

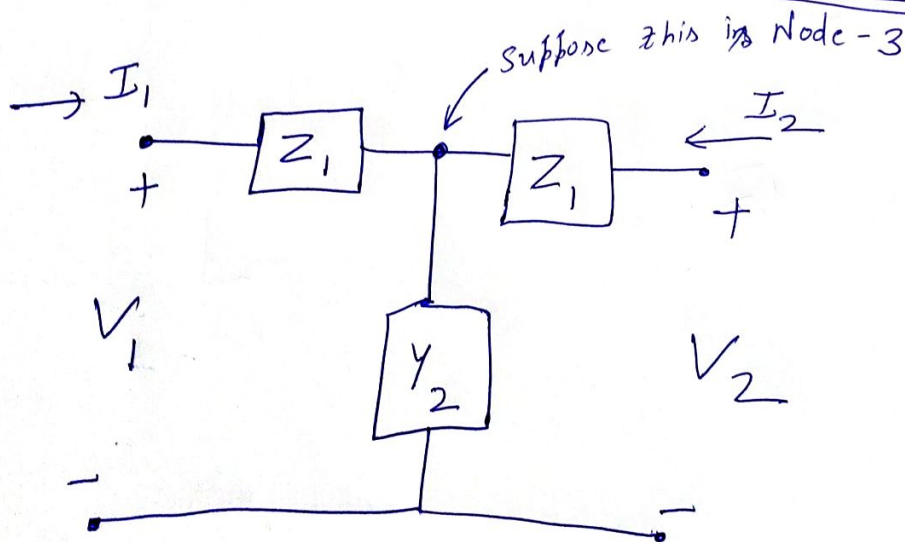

⇒ Here, we have two series impedance Z_1 and a shunt admittance Y_2 .

At Node-3

$$\frac{V_3 - 0}{Y_2} = \frac{V_1 - V_3}{Z_1} + \frac{V_2 - V_3}{Z_1}$$

↳ So, we can easily solve it.

2) \Rightarrow But ~~instead~~ ^{instead} of solving this by traditional ~~method~~ method, we will use ABCD matrix of series element & shunt element.

Step-1 In this circuit we have 3 different -
Circuit elements. So, we will divide this network into 3 different networks.

Step-2

~~ABC~~

For series,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \quad (\text{lecture } -3)$$

For shunt,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \quad (\text{lecture } -4)$$

So, here in this network we have two series networks and one shunt network.
 \Rightarrow So, just multiply these matrix one by one.

③

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ y_2 & 1 \end{bmatrix} \begin{bmatrix} 1 & z_1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + z_1 y_2 & z_1 \\ y_2 & 1 \end{bmatrix} \begin{bmatrix} 1 & z_1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + z_1 y_2 & z_1 + z_1^2 y_2 + z_1 \\ y_2 & y_2 z_1 + 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + z_1 y_2 & z_1 + z_1^2 y_2 \\ y_2 & 1 + y_2 z_1 \end{bmatrix}$$

↳ This is ABCD matrix of a cascaded network.

↳ Advantage of this approach is that we can easily find relation b/w i/p & o/p voltage and current with the help of this ABCD matrix.

(7)
=

Note:- Like other networks, the cascaded network consisting of impedance & admittance should be symmetrical & reciprocal.

⇒ So, we can easily check whether ~~our~~ answer is correct or not.

⇒ The ABCD matrix of cascaded network is,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + Z_1 Y_2 & 2Z_1 + Z_1^2 Y_2 \\ Y_2 & 1 + Y_2 Z_1 \end{bmatrix}$$

Here, $A = D$ \therefore network is symmetrical.

We know that,

For reciprocal network,

$$AD - BC = 1$$

$$\therefore (1 + Z_1 Y_2) (1 + Y_2 Z_1)$$

$$- (2Z_1 + Z_1^2 Y_2) (Y_2)$$


$$= 1 + Y_2 Z_1 + Z_1 Y_2 + Y_2^2 Z_1^2 - 2Z_1 Y_2 - Z_1^2 Y_2^2$$

= 1 (Hence, reciprocal network also).

5)

⇒ Thus our ABCD matrix is correct because the network is both symmetrical & reciprocal.


Some additional information

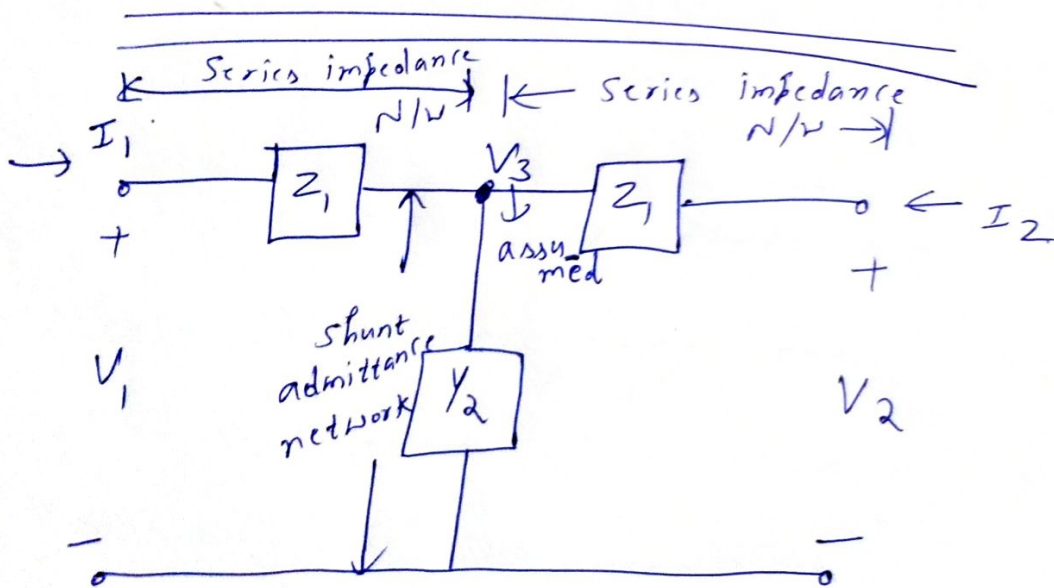

⇒ So, in this approach we have divided this network into three different networks.


⇒ Suppose current I_1 is entering series impedance network on the left side. (Z_1)

⇒

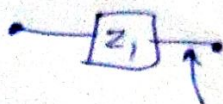

Current here will be (-)ve

6

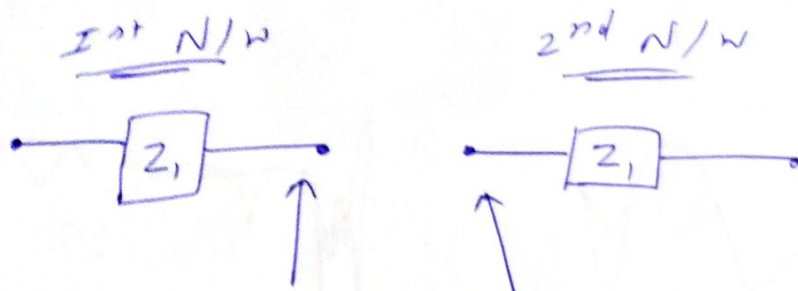

Current here will be (-)ve

But the same current will be (+)ve here as it is at the i/P port of second series impedance n/w.

⇒ So, we can say that whatever current will be going out will become i/P voltage & i/P current over other network.

⇒ So, these ABCD matrix can be (Z_1) of first network

multiplied with ABCD matrix of shunt network (Y_1) .

And then with ABCD matrix of series impedance network on right side.